

Statement of Problem 4.4-7 page 145

$$\text{MTX}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \begin{pmatrix} -1 & \frac{K_{IV}}{R_B} + 1 & 0 & 0 & 0 \\ K_{VV} & -1 - \frac{K_{IV}}{R_B} & 0 & 0 & 0 \\ \frac{-1}{R_A} & 0 & 1 & 1 & 0 \\ \frac{1}{R_A} & \frac{1}{R_B} & 0 & 0 & -1 \\ 0 & \frac{-1}{R_B} - \frac{1}{R_D} & 0 & -1 & 0 \end{pmatrix} \begin{matrix} \text{Loop 2} \\ \text{Loop 3} \\ \text{Node 1} \\ \text{Node 2} \\ \text{Node 3} \end{matrix}$$

Vector-Matrix solution of problem

$$\text{VectS}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \text{MTX}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)^{-1} \cdot \begin{bmatrix} -\frac{K_{IV}}{R_B} \cdot V_S \\ \left(\frac{K_{IV}}{R_B} - K_{VV} \right) \cdot V_S \\ \frac{V_S}{R_A} \\ -\left(\frac{1}{R_A} + \frac{1}{R_B} \right) \cdot V_S \\ \frac{V_S}{R_B} \end{bmatrix}$$

Functional extraction of each unknown from the vector solution (inefficient but simple)

$$VS_1(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \text{VectS}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)0$$

$$VS_3(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \text{VectS}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)1$$

$$IVVS(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \text{VectS}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)2$$

$$IIVS(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \text{VectS}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)3$$

$$ICS(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) := \text{VectS}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)4$$

The known parameters as stated in Problem 4.4-7 page 145

$V_S := -15$	$K_{IV} := 10$	$K_{VV} := 4$	$R_A := 10$	$R_B := 20$	$R_D := 5$	New values
$V_S := -10$	$K_{IV} := 8$	$K_{VV} := 3$	$R_A := 2$	$R_B := 8$	$R_D := 4$	Problem statement
						Place active ones here

First, check the determinant to make sure that we don't have a redundant equation or trick problem.

$$|\text{MTX}(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)| = 4$$

Store the output in scalar variables

$$V_1 := VS_1(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) \quad V_3 := VS_3(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)$$

$$I_{VV} := IVVS(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D) \quad I_{IV} := IIVS(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)$$

$$I_C := ICS(V_S, K_{IV}, K_{VV}, R_A, R_B, R_D)$$

Compute all the other parameters for the solution from the outputs

$$V_B := V_3 + V_S \quad V_A := V_1 + V_S \quad V_2 := -V_S \quad V_D := V_3$$

$$I_A := \frac{V_A}{R_A} \quad I_B := \frac{V_B}{R_B} \quad I_D := \frac{V_D}{R_D}$$

Give the solution numerically

$$V_A = 5 \quad V_B = 2.5 \quad V_D = 12.5$$

$$I_A = 2.5 \quad I_B = 0.312 \quad I_D = 3.125$$

$$V_1 = 15 \quad V_2 = 10 \quad V_3 = 12.5$$

$$I_{VV} = 5.937 \quad I_{IV} = -3.437 \quad I_C = 2.813$$

Checks

$$\text{Loop 1:} \quad V_B - V_D - V_S = 0$$

$$\text{Loop 2:} \quad K_{IV} \cdot I_B + V_B - V_A = 0$$

$$\text{Loop 3:} \quad -V_D - K_{IV} \cdot I_B + K_{VV} \cdot V_A = -7.105 \times 10^{-15}$$

$$\text{Node 1:} \quad I_{VV} + I_{IV} - I_A = 0$$

$$\text{Node 2:} \quad I_A + I_B - I_C = -1.776 \times 10^{-15}$$

$$\text{Node 3:} \quad -I_{IV} - I_B - I_D = 0$$