

The Problem Solving Method using Kirchoff's Laws

Loop 1

$$-v_s + v_a + v_c = 0$$

Loop 2

$$-v_c + v_b + v_{is} = 0$$

Node 1

$$i_{vs} - i_a = 0$$

Node 2

$$i_a - i_c - i_b = 0$$

Node 3

$$i_b + i_s = 0$$

Node 4 is redundant with Node 1, Node 2, and Node 3 (Why?)

$$-i_{vs} + i_c - i_s = 0$$

Ohm's Law for R.a

$$v_a = i_a \cdot R_a$$

Ohm's Law for R.b

$$v_b = i_b \cdot R_b$$

Ohm's Law for R.c

$$v_c = i_c \cdot R_c$$

Sources are v_s and i_s

Unknowns are i_{vs} , v_{is} , and the voltages and currents across the resistors.

Arranging the equations as a vector-matrix equation:

$$\begin{pmatrix} 0 & 0 & 1 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & -1 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & -R_a & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -R_b & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -R_c \end{pmatrix} \cdot \begin{pmatrix} i_{vs} \\ v_{is} \\ v_a \\ v_b \\ v_c \\ i_a \\ i_b \\ i_c \end{pmatrix} = \begin{pmatrix} v_s \\ 0 \\ 0 \\ 0 \\ i_s \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

The solution, using matrix notation:

$$\text{soln}(v_s, i_s, R_a, R_b, R_c) := \begin{pmatrix} 0 & 0 & 1 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & -1 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & -R_a & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -R_b & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -R_c \end{pmatrix}^{-1} \begin{pmatrix} v_s \\ 0 \\ 0 \\ 0 \\ i_s \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\text{soln}(12, .01, 10000, 22000, 12000) = \begin{pmatrix} -4.909 \times 10^{-3} \\ 281.091 \\ -49.091 \\ -220 \\ 61.091 \\ -4.909 \times 10^{-3} \\ -0.01 \\ 5.091 \times 10^{-3} \end{pmatrix}$$

For trial values as given

$$\text{soln}(12, .001, 10000, 22000, 12000) = \begin{pmatrix} 0 \\ 34 \\ 0 \\ -22 \\ 12 \\ 0 \\ -1 \times 10^{-3} \\ 1 \times 10^{-3} \end{pmatrix} \quad \text{Change i.s to 1 ma}$$

An algebraic solution

$$\begin{pmatrix} 0 & 0 & 1 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & -1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & -1 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & -R_a & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -R_b & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -R_c \end{pmatrix}$$

by matrix inversion, yields

[OMITTED LARGE EQUATION]

simplifies to

$$\left[\begin{array}{cccccccc} \frac{1}{R_c + R_a} & 0 & 1 & \frac{R_c}{R_c + R_a} & \frac{-R_c}{R_c + R_a} & \frac{-1}{R_c + R_a} & 0 & \frac{-1}{R_c + R_a} \\ \frac{R_c}{R_c + R_a} & 1 & 0 & (-R_a) \cdot \frac{R_c}{R_c + R_a} & \frac{R_c \cdot R_b + R_a \cdot R_c + R_a \cdot R_b}{R_c + R_a} & \frac{-R_c}{R_c + R_a} & -1 & \frac{R_a}{R_c + R_a} \\ \frac{R_a}{R_c + R_a} & 0 & 0 & R_a \cdot \frac{R_c}{R_c + R_a} & (-R_a) \cdot \frac{R_c}{R_c + R_a} & \frac{R_c}{R_c + R_a} & 0 & \frac{-R_a}{R_c + R_a} \\ 0 & 0 & 0 & 0 & -R_b & 0 & 1 & 0 \\ \frac{R_c}{R_c + R_a} & 0 & 0 & (-R_a) \cdot \frac{R_c}{R_c + R_a} & R_a \cdot \frac{R_c}{R_c + R_a} & \frac{-R_c}{R_c + R_a} & 0 & \frac{R_a}{R_c + R_a} \\ \frac{1}{R_c + R_a} & 0 & 0 & \frac{R_c}{R_c + R_a} & \frac{-R_c}{R_c + R_a} & \frac{-1}{R_c + R_a} & 0 & \frac{-1}{R_c + R_a} \\ 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ \frac{1}{R_c + R_a} & 0 & 0 & \frac{-R_a}{R_c + R_a} & \frac{R_a}{R_c + R_a} & \frac{-1}{R_c + R_a} & 0 & \frac{-1}{R_c + R_a} \end{array} \right] \cdot \frac{R_c + R_a}{R_c \cdot R_a}$$

simplifies to

$$\left[\begin{array}{cccccccc} \frac{1}{R_a \cdot R_c} & 0 & \frac{R_c + R_a}{R_a \cdot R_c} & \frac{1}{R_a} & \frac{-1}{R_a} & \frac{-1}{R_a \cdot R_c} & 0 & \frac{-1}{R_a \cdot R_c} \\ \frac{1}{R_a} & \frac{R_c + R_a}{R_a \cdot R_c} & 0 & -1 & \frac{R_c \cdot R_b + R_a \cdot R_c + R_a \cdot R_b}{R_a \cdot R_c} & \frac{-1}{R_a} & \frac{-(R_c + R_a)}{R_a \cdot R_c} & \frac{1}{R_c} \\ \frac{1}{R_c} & 0 & 0 & 1 & -1 & \frac{1}{R_a} & 0 & \frac{-1}{R_c} \\ 0 & 0 & 0 & 0 & (-R_b) \cdot \frac{R_c + R_a}{R_a \cdot R_c} & 0 & \frac{R_c + R_a}{R_a \cdot R_c} & 0 \\ \frac{1}{R_a} & 0 & 0 & -1 & 1 & \frac{-1}{R_a} & 0 & \frac{1}{R_c} \\ \frac{1}{R_a \cdot R_c} & 0 & 0 & \frac{1}{R_a} & \frac{-1}{R_a} & \frac{-1}{R_a \cdot R_c} & 0 & \frac{-1}{R_a \cdot R_c} \\ 0 & 0 & 0 & 0 & \frac{-(R_c + R_a)}{R_a \cdot R_c} & 0 & 0 & 0 \\ \frac{1}{R_a \cdot R_c} & 0 & 0 & \frac{-1}{R_c} & \frac{1}{R_c} & \frac{-1}{R_a \cdot R_c} & 0 & \frac{-1}{R_a \cdot R_c} \end{array} \right] \begin{pmatrix} v_s \\ 0 \\ 0 \\ 0 \\ 0 \\ i_s \\ 0 \\ 0 \end{pmatrix}$$

simplifies to

$$\left[\begin{array}{c}
 \frac{-[(-v_s) + i_s \cdot R_c]}{R_a \cdot R_c} \\
 \frac{v_s \cdot R_c + i_s \cdot R_c \cdot R_b + i_s \cdot R_a \cdot R_c + i_s \cdot R_a \cdot R_b}{R_a \cdot R_c} \\
 \frac{-[(-v_s) + i_s \cdot R_c]}{R_c} \\
 (-R_b) \cdot \frac{R_c + R_a}{R_a \cdot R_c} \cdot i_s \\
 \frac{v_s + i_s \cdot R_a}{R_a} \\
 \frac{-[(-v_s) + i_s \cdot R_c]}{R_a \cdot R_c} \\
 [-(R_c + R_a)] \cdot \frac{i_s}{R_a \cdot R_c} \\
 \frac{v_s + i_s \cdot R_a}{R_a \cdot R_c}
 \end{array} \right] \cdot \frac{R_c \cdot R_a}{R_c + R_a}$$

simplifies to

$$\left[\begin{array}{c}
 \frac{-[(-v_s) + i_s \cdot R_c]}{R_c + R_a} \\
 \frac{v_s \cdot R_c + i_s \cdot R_c \cdot R_b + i_s \cdot R_a \cdot R_c + i_s \cdot R_a \cdot R_b}{R_c + R_a} \\
 [-[(-v_s) + i_s \cdot R_c]] \cdot \frac{R_a}{R_c + R_a} \\
 (-R_b) \cdot i_s \\
 (v_s + i_s \cdot R_a) \cdot \frac{R_c}{R_c + R_a} \\
 \frac{-[(-v_s) + i_s \cdot R_c]}{R_c + R_a} \\
 -i_s \\
 \frac{v_s + i_s \cdot R_a}{R_c + R_a}
 \end{array} \right]$$